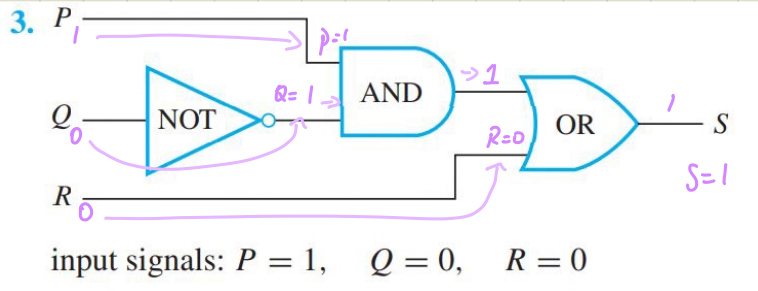


Susanna 76  $\rightarrow 3, 4, 7, 8, 11$

Fig 76:  $\{3, 4, 7, 8, 11\}$

Give Output signals




Find the Boolean expression of:

⑪ Exercise 3

$$\begin{aligned} P &= 1 & P \wedge Q &= 1 \\ Q &= 0 \\ R &= 0 \end{aligned}$$

$$(P \wedge Q) \vee (R) = 1$$

$$P \wedge Q \vee R$$

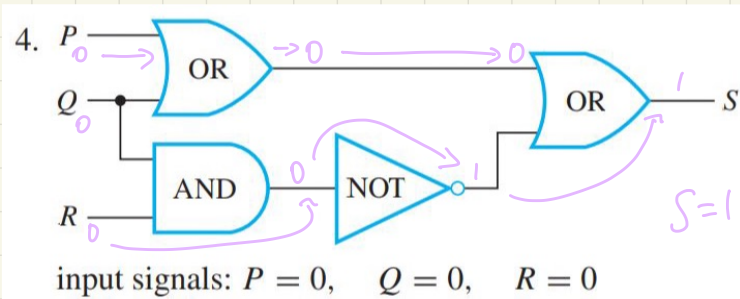

⑫ Exercise 4

$$\begin{aligned} P &= 0 & P \vee Q &= 0 & (P \wedge Q) \vee (\neg(Q \wedge R)) &= 1 \\ Q &= 0 \\ R &= 0 & Q \wedge R &= 0 & \neg(Q \wedge R) &= 1 \end{aligned}$$

$$(P \wedge Q) \vee (\neg(Q \wedge R))$$

Write I/O table for

⑦ Exercise 3:

P	Q	R	$\neg Q$	$(P \wedge \neg Q)$	$(P \wedge \neg Q) \vee R$
T	T	T	F	F	T
T	T	F	F	F	F
T	F	T	T	T	T
T	F	F	T	T	T
F	T	T	F	F	T
F	T	F	F	F	F
F	F	T	T	F	T
F	F	F	T	F	F


⑧ Exercise 4

P	Q	R	$\neg Q$	$P \vee Q$	$Q \wedge R$	$\neg(Q \wedge R)$	$(P \vee Q) \vee (\neg(Q \wedge R))$
T	T	T	F	T	T	F	T
T	T	F	F	T	F	T	T
T	F	T	T	T	F	T	T
T	F	F	T	T	F	T	T
F	T	T	F	T	T	F	T
F	T	F	F	T	F	T	T
F	F	T	T	F	F	T	T
F	F	F	T	F	F	T	F

Page 76 {17, 19, 28, 31, 34}

Construct Circuits for

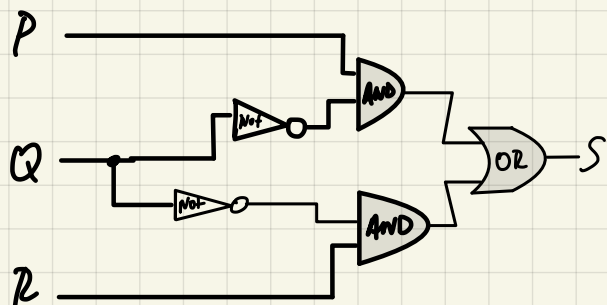(17)  $(P \wedge \neg Q) \vee (\neg P \wedge R)$




Construct a Boolean expression and circuit for:

$$S = (P \wedge Q \wedge \neg R) \vee (P \wedge \neg Q \wedge \neg R) \vee (\neg P \wedge Q \wedge \neg R)$$



(19)

P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	0
0	0	0	0

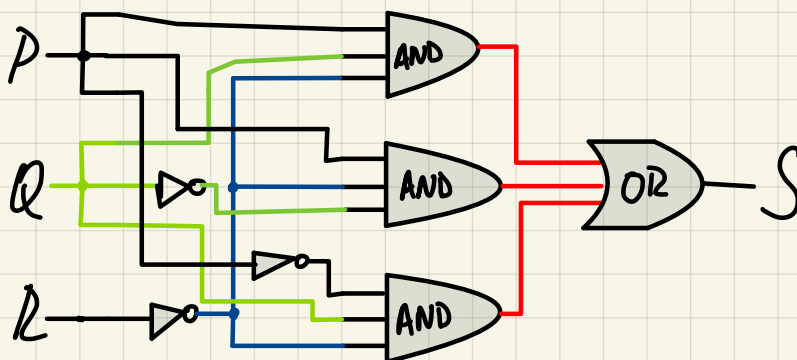$\rightarrow P \wedge Q \wedge \neg R$   
 $\rightarrow P \wedge \neg Q \wedge \neg R$   
 $\sim P \wedge Q \wedge \neg R$



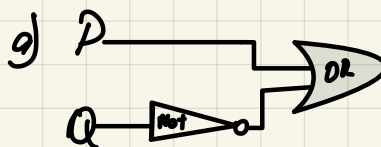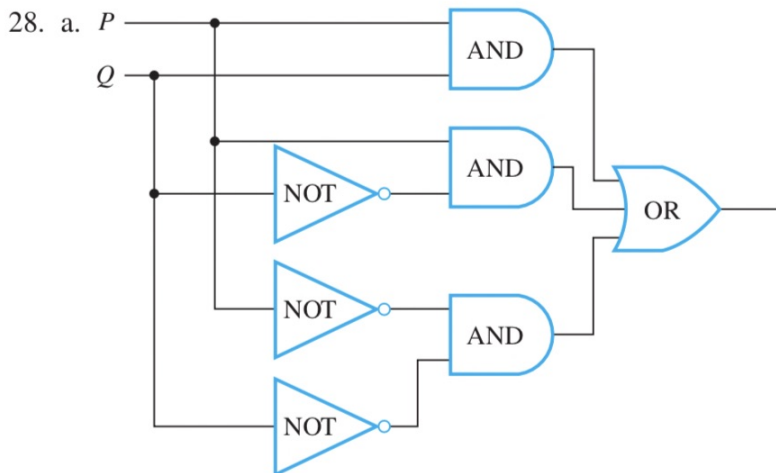Use the properties listed in Theorem 2.1.1 to show that each pair of circuits in 26–29 have the same input/output table. (Find the Boolean expressions for the circuits and show that they are logically equivalent when regarded as statement forms.)




$$\begin{aligned}
 & (P \wedge Q) \vee (P \wedge \neg Q) \vee (\neg P \wedge \neg Q) \\
 \equiv & (P \wedge Q) \vee (P \wedge \neg Q) \vee (\neg P \wedge \neg Q) \leftarrow \text{Associative} \\
 \equiv & (P \wedge (Q \vee \neg Q)) \vee (\neg P \wedge \neg Q) \leftarrow \text{Distributive} \\
 \equiv & (P \wedge T) \vee (\neg P \wedge \neg Q) \leftarrow \text{Negation} \\
 \equiv & P \vee (\neg P \wedge \neg Q) \leftarrow \text{Identity} \\
 \equiv & (P \vee \neg P) \wedge (P \vee \neg Q) \leftarrow \text{Distributive} \\
 \equiv & T \wedge (P \vee \neg Q) \leftarrow \text{Negation} \\
 \equiv & (P \vee \neg Q) \wedge T \leftarrow \text{Commutative} \\
 \equiv & P \vee \neg Q \leftarrow \text{Identity}
 \end{aligned}$$

$$(P \wedge Q) \vee (P \wedge \neg Q) \vee (\neg P \wedge \neg Q) \equiv P \vee \neg Q$$

For the circuits corresponding to the Boolean expressions in each of 30 and 31 there is an equivalent circuit with at most two logic gates. Find such a circuit.
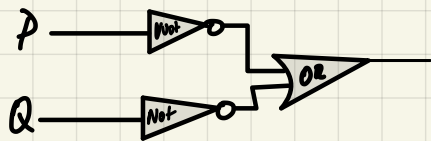
$$(31) (\sim P \wedge \sim Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q)$$



(34) Show that the following logical equivalences hold for the Pierce arrow  $\downarrow$ , where  $P \downarrow Q \equiv \sim(P \vee Q)$

$$c) P \wedge Q \equiv (P \downarrow P) \downarrow (Q \vee Q)$$

$$\begin{aligned}
 P \wedge Q &\equiv (P \downarrow P) \downarrow (Q \vee Q) \\
 &\equiv \sim(\sim(P \vee P)) \vee \sim(Q \vee Q) \rightarrow \text{Definition of } \downarrow \\
 &\equiv \sim(\sim(P \vee P)) \wedge \sim(\sim(Q \vee Q)) \rightarrow \text{De Morgan's Law} \\
 &\equiv (P \vee P) \wedge (Q \vee Q) \rightarrow \text{Double Complementation} \\
 &\equiv P \wedge Q \rightarrow \text{Idempotent Law}
 \end{aligned}$$